

Download this and other FREE materials from <https://teacher.co.ke/notes>

1. Name a property of light that shows it is a transverse wave. (1mk)

polarization =

2. State THREE differences between light waves and sound waves. (3mk)

✓ light waves are longitudinal transverse	sound is a longitudinal wave
✓ light is an electromagnetic wave	sound is a mechanical wave
sound can light moves only in a straight line	- sound can be bend over obstacles.


3. Explain why radio wave signals are easier to receive than TV waves signals in a place surrounded by hills. (2mk)

They have a longer wavelength than radio waves so they can easily go over obstacles.

4. When a sound wave travels from a dense to a less dense gas, its velocity changes. What wave property does this observation show? Explain your answer. (3mk)

✓ Refraction of sound.
✓ Refraction is caused by change in velocity which leads to change in direction.

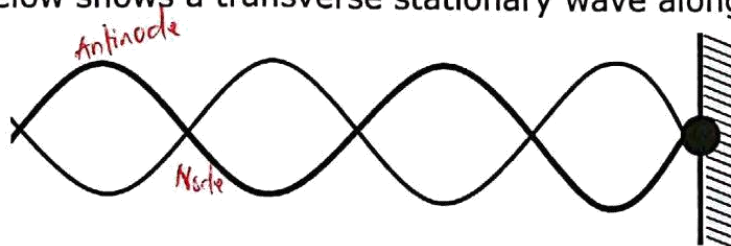5. The figure below shows a transverse stationary wave along a string.



- i) Label the nodes and antinodes. (1mk)
- ii) If the distance between an antinode and a node is **0.08m**, determine the wavelength of the wave of the stationary wave (2mk)

$$\lambda = 0.08 \times 4 = \underline{\underline{0.32\text{m}}}$$

- iii) State one factor which does not change as water waves move from shallow to deep end (1mk)

frequency

- iv) What is meant by the term interference as applied to waves. (1mk)

A phenomenon ~~is~~ that occurs when two waves merge

- v) Explain the meaning of coherent source of wave. (1mk)

These are waves of similar frequency and ~~and~~ having constant ~~is~~ phase difference.

6. An electric heater is found to have a resistance of **950Ω** when operating normally on a **240V** mains. Find the power rating of the heater. (2mk)

$$P = \frac{V^2}{R} = \frac{240^2}{950} = 60.63 \text{ W}$$

7. An electric bulb rated **40W** is operating on **240V** mains. Determine the resistance of its filament (3mk)

$$P = \frac{V^2}{R}$$

$$40 = \frac{240^2}{R}$$

$$R = \frac{240^2}{40}$$

$$R = 1440 \Omega$$

8. When a current of **2A** flows in a resistor for **10** minutes, **15kJ** of electrical energy is dissipated. Determine the voltage across the resistor. (3mk)

$$E = VI t$$

$$\frac{15000}{1200} = \frac{V \times 2 \times 600}{1200}$$

$$V = 12.5 \text{ V}$$

9. An electric bulb with a filament of resistance **480Ω** is connected to a **240V** mains supply. Determine the energy dissipated in **2** minutes. (3mk)

$$\begin{aligned} R &= 480 \Omega \\ V &= 240 \text{ V} \\ t &= 2 \text{ min} = 120 \text{ s} \end{aligned} \left\{ \begin{aligned} E &= \frac{V^2}{R} t \\ &= \frac{240^2}{480} \times 120 \end{aligned} \right\} E = 14400 \text{ J}$$

10. Two electric heaters A and B rated 1000 W and 2500 W respectively are connected in parallel across a 240 mains supply. Calculate the ratio $R_A : R_B$ of their resistances. (3mks)

$$R_A = \frac{V^2}{P_A} = \frac{240^2}{1000} = 57.6$$

$$R_B = \frac{V^2}{P_B} = \frac{240^2}{2500} = 23.04$$

$$R_A : R_B = 57.6 : 23.04$$

$$R_A : R_B = 5 : 2$$


11. Two capacitors of capacitance **2μF** and **1μF** are connected in parallel. A p.d of 3V is applied across them. Find the energy stored in the combination. (3mk)

$$E = \frac{1}{2} C V^2$$

$$= \frac{1}{2} \times 3 \times 3^2 \times 10^{-6}$$

$$E = 1.35 \times 10^{-5} \text{ J}$$

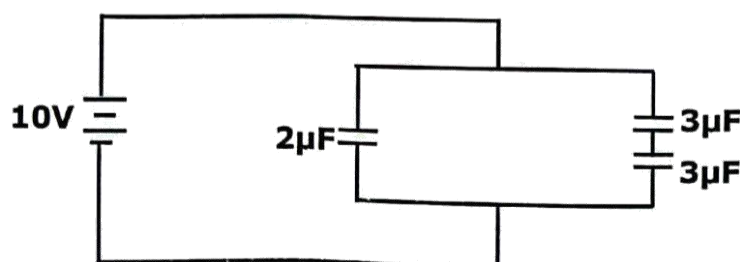12. The fig. shows an arrangement of capacitors connected to a 10v. D.C supply determine:-



- i) The charge stored in the $2\mu\text{F}$ capacitor. (2mk)


$$Q = CV$$

$$= 2 \times 10 = 20\mu\text{C}$$

- ii) The total capacitance of the arrangement. (2mk)

$$C_T = \left(\frac{3 \times 3}{3+3} \right) + 2 = 3.5\mu\text{F}$$

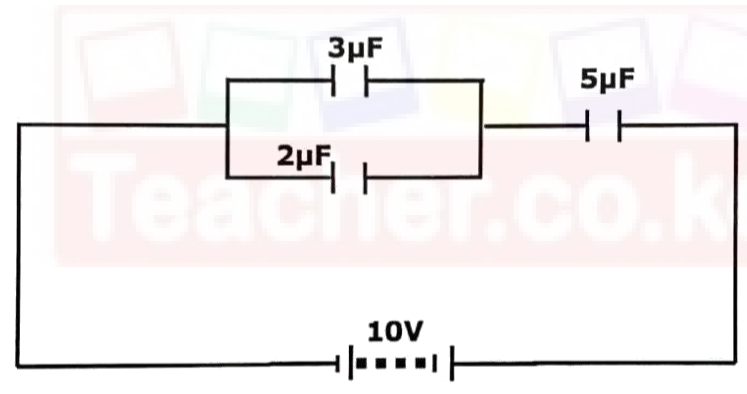13. Figure shows a circuit diagram with three capacitors.



- (i) Determine the effective capacitance. (3mk)

~~$$C_T = \frac{3 \times 2}{3+2} = 1.2\mu\text{F}$$~~

$$C_T = \frac{(3+2) \times 5}{10} = 2.5\mu\text{F}$$

(3mk)

- (ii) Find the charge on the $3\mu\text{F}$

$$Q = CV$$

$$= 10 \times 2.5$$

$$= 25\mu\text{C}$$

$$V = \frac{Q}{C}$$

$$= \frac{25}{5} = 5\text{V}$$

$$10 - 5 = 5\text{V}$$

$$Q = CV = 3 \times 5 = 15\mu\text{C}$$

14. A crane lifts a load of **500 kg** through a vertical distance of **2m** in **8 s** determine

- i) Work done by the crane (2mk)

$$Wd = mgh \\ = 500 \times 10 \times 2 = 10,000 \text{ J}$$

- ii) Power developed by the crane (2mk)

$$P = \frac{E}{t} = \frac{10,000}{8} = \underline{\underline{1,250 \text{ J/s}}}$$

- iii) Efficiency of the crane given that its operated by all electric motor rated **2kW** (2mk)

$$\eta = \frac{P_{out}}{P_{input}} \times 100 = \frac{1250}{2000} \times 100 = \underline{\underline{62.5\%}}$$

b) State two effects which contribute to the efficiency being less than 100% (2mk)

- ✓ The machine carries its own weight.
- ✓ friction between moving parts.